

## Set 5, Part 1: Symbolic Algebra with *Mathematica*

To explore the functionality of *Mathematica*, I'll use it to solve a problem from my Ph1c set last week.

Consider a circuit with a battery of voltage  $V$ , resistor with resistance  $R$ , and inductor with inductance  $L$  in series. The voltage around the single loop must sum to 0, which gives us an ODE for the current  $j$ :

In[72]:= **ODE** = { $V - j[t] R - j'[t] L == 0$ }

Out[72]=  $\{-L j'(t) - R j(t) + V == 0\}$

In[73]:= **DSolve**[**ODE**, { $j[t]$ }, { $t$ }]

Out[73]=  $\left\{ \left\{ j(t) \rightarrow c_1 e^{-\frac{R t}{L}} + \frac{V}{R} \right\} \right\}$

We define a function for the current  $J(t)$  according to this solution:

In[74]:= **J**[ $t\_$ ] :=  $c_1 e^{-\frac{R t}{L}} + \frac{V}{R}$

We know that at  $t = 0$ , the inductor will fight the current change completely. Thus,  $J(0) = 0$ .

In[75]:= **Solve**[**J**[0] == 0, { $c_1$ }]

Out[75]=  $\left\{ \left\{ c_1 \rightarrow -\frac{V}{R} \right\} \right\}$

Now that we have the complete solution, let us store it as the actual current  $i(t)$ :

In[76]:= **i**[ $t\_$ ] = **J**[ $t$ ] /.  $c_1 \rightarrow -\frac{V}{R}$

Out[76]=  $\frac{V}{R} - \frac{V e^{-\frac{R t}{L}}}{R}$

Now suppose we allow the circuit to run until some time  $T$ . To calculate the energy delivered by the battery over this time, we integrate power:

In[77]:= **batE** =  $\int_0^T i[t] V dt$

Out[77]=  $\frac{V^2 \left( L \left( e^{-\frac{R T}{L}} - 1 \right) + R T \right)}{R^2}$

The energy stored in the inductor at time  $T$  is simply:

In[78]:= **inductorE** =  $\frac{1}{2} L (i[T])^2$

Out[78]=  $\frac{1}{2} L \left( \frac{V}{R} - \frac{V e^{-\frac{R T}{L}}}{R} \right)^2$

And the energy dissipated by the resistor over time is also obtained from integrating power. However, the resistor's voltage changes over time:

$$\text{In[79]:= resistorE} = \int_0^T (\text{i[t]})^2 R \, dt$$

$$\text{Out[79]= } \frac{V^2 \left( L e^{-\frac{2RT}{L}} \left( 4 e^{\frac{RT}{L}} - 1 \right) - 3L + 2RT \right)}{2R^2}$$

We confirm that energy was conserved:

$$\text{In[80]:= Ediff} = \text{batE} - (\text{inductorE} + \text{resistorE})$$

$$\text{Out[80]= } \frac{V^2 \left( L \left( e^{-\frac{RT}{L}} - 1 \right) + RT \right)}{R^2} - \frac{V^2 \left( L e^{-\frac{2RT}{L}} \left( 4 e^{\frac{RT}{L}} - 1 \right) - 3L + 2RT \right)}{2R^2} - \frac{1}{2} L \left( \frac{V}{R} - \frac{V e^{-\frac{RT}{L}}}{R} \right)^2$$

$$\text{In[81]:= Simplify[Ediff]}$$

$$\text{Out[81]= } 0$$